



Virtual University

About Us

CS302
Solved Final Terms Papers

Waqar.siddhu@gmail.com

Year
2017

For More Plz Visit

WWW.VirtualAcademyLive.com

بِسْمِ اللَّهِ الرَّحْمَنِ الرَّحِيمِ

In the Name of Allāh, the Most Gracious, the Most Merciful

Paper Pattern

MCQS 40 each 1 mark
Short 4 each 2 marks
Short 4 each 3 marks
long 4 each 5 marks

Question No : 1 of 52	Marks: 1 (Budgeted Time 1 Min)
Excess-8 code assigns _____ to "-8"	
Answer (Please select your correct option)	
<input type="radio"/> 1110	WWW.VirtualAcademyLive.com
<input type="radio"/> 1100	
<input type="radio"/> 1000	
<input type="radio"/> 0000	
correct	
Made by: Waqar Siddhu	
Question No : 2 of 52	Marks: 1 (Budgeted Time 1 Min)
The Extended ASCII Code (American Standard Code for Information Interchange) represents _____ unique codes	
Answer (Please select your correct option)	
<input type="radio"/> 256	WWW.VirtualAcademyLive.com
<input type="radio"/> 255	
<input type="radio"/> 128	
<input type="radio"/> 127	
correct	
Made by: Waqar Siddhu	

Question No : 3 of 52

Marks: 1 (Budgeted Time 1 Min)

The 3-variable Karnaugh Map (K-Map) has _____ cells for min or max terms

Answer (Please select your correct option)

WWW.VirtualAcademyLive.com

☐ 4

☐ 8

☐ 12

☐ 16

correct

Made by: Waqar Siddhu

Question No : 4 of 52

Marks: 1 (Budgeted Time 1 Min)

The active high and active low inputs of 3-to-8 Decoder are as follows:

Answer (Please select your correct option)

WWW.VirtualAcademyLive.com

☐ One active-high and the remaining two are active-low.

correct

☐ Two active-high and the remaining one is active-low.

☐ All active high

☐ All active low

Made by: Waqar Siddhu

Question No : 5 of 52

Marks: 1 (Budgeted Time 1 Min)

Two 2-input, 4-bit multiplexers 74X157 can be connected to implement a ____ multiplexer.

Answer (Please select your correct option)

WWW.VirtualAcademyLive.com

☐ 2-input, 4-bit

☐ 4-input, 8-bit

☐ 4-input, 16-bit

☐ 2-input, 8-bit

correct

Made by: Waqar Siddhu

Question No : 6 of 52

Marks: 1 (Budgeted Time 1 Min)

GAL is an acronym for _____.

Answer (Please select your correct option)

WWW.VirtualAcademyLive.com

☐ Generic Analysis Logic

☐ Giant Array Logic

☐ General Array Logic

☐ Generic Array Logic

correct

Made by: Waqar Siddhu

Question No : 7 of 52

Marks: 1 (Budgeted Time 1 Min)

74HC163 has two enable input pins which are _____ and _____.

Answer (Please select your correct option)

WWW.VirtualAcademyLive.com

☐ ENP, ENT

correct

☐ ENI, ENC

☐ ENP, ENC

☐ ENT, ENI

Made by: Waqar Siddhu

Question No : 8 of 52

Marks: 1 (Budgeted Time 1 Min)

$A.(B + C) = AB + A.C$ is an expression of _____.

Answer (Please select your correct option)

WWW.VirtualAcademyLive.com

☐ Demorgan's Law

☐ Commutative Law

☐ Distributive Law

correct

☐ Associative Law

Made by: Waqar Siddhu

Question No : 9 of 52

Marks: 1 (Budgeted Time 1 Min)

An 8-bit serial in / parallel out shift register contains the value "8", _____ clock signal(s) will be required to shift the value completely out of the register.

Answer (Please select your correct option)

WWW.VirtualAcademyLive.com

1

☐

correct

2

☐

4

☐

8

☐

Made by: Waqar Siddhu

Question No : 10 of 52

Marks: 1 (Budgeted Time 1 Min)

2's complement of -5 is _____

Answer (Please select your correct option)

WWW.VirtualAcademyLive.com

1000

☐

1011

☐

correct

1100

☐

1110


☐

Made by: Waqar Siddhu

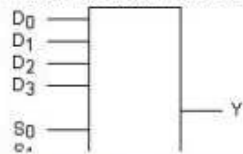Question No : 11 of 52

Marks: 1 (Budgeted Time 1 Min)

The device shown here is most likely a _____



Answer (Please select your correct option)

WWW.VirtualAcademyLive.com

Comparator

☐

Multiplexer

☐

correct

Demultiplexer

☐

Parity generator

☐

Made by: Waqar Siddhu

Question No : 12 of 52

Marks: 1 (Budgeted Time 1 Min)

What will be output state when $J = 1$, $K = 0$ and CLR input is active?

Answer (Please select your correct option)

WWW.VirtualAcademyLive.com

☐ Q = 1

correct

☐ Q = 0

☐ Retains previous output state

☐ Toggle output

Made by: Waqar Siddhu

Question No : 13 of 52

Marks: 1 (Budgeted Time 1 Min)

Which of the following statement is true?

Answer (Please select your correct option)

WWW.VirtualAcademyLive.com

☐ Power consumption of TTL is higher than CMOS

correct

☐ Power consumption of CMOS is higher than TTL

☐ Both TTL and CMOS have same power consumption

☐ Power consumption of both CMOS and TTL depends on number of gates in the circuit.

Made by: Waqar Siddhu

Question No : 14 of 52

Marks: 1 (Budgeted Time 1 Min)

_____ counters as the name indicates are not triggered simultaneously.

Answer (Please select your correct option)

WWW.VirtualAcademyLive.com

☐ Synchronous

☐ Asynchronous

correct

☐ Positive-Edge triggered

☐ Negative-Edge triggered

Made by: Waqar Siddhu

Question No : 15 of 52

Marks: 1 (Budgeted Time 1 Min)

_____ is said to occur when multiple internal variables change due to change in one input variable.

Answer (Please select your correct option)

WWW.VirtualAcademyLive.com

☐ Race condition

correct

☐ Propagation delay

☐ Ripple effect

☐ Clock skew

Made by: Waqar Siddhu

Question No : 16 of 52

Marks: 1 (Budgeted Time 1 Min)

A 5-bit counter has a maximum _____ modulus.

Answer (Please select your correct option)

WWW.VirtualAcademyLive.com

☐ 10

☐ 16

☐ 25

☐ 32

correct

Made by: Waqar Siddhu

Question No : 17 of 52

Marks: 1 (Budgeted Time 1 Min)

The Sequential circuit whose output depends on the current state and the input is known as _____.

Answer (Please select your correct option)

WWW.VirtualAcademyLive.com

☐ Moore Machine

☐ Mealy Machine

correct

☐ Counter

☐ Flip Flop

Made by: Waqar Siddhu

Question No : 18 of 52

Marks: 1 (Budgeted Time 1 Min)

In _____, the \bar{Q} output of the last flip-flop of the shift register is connected to the data input of the first flip-flop.

Answer (Please select your correct option)

WWW.VirtualAcademyLive.com

☐ Moore machine☐ Mealy machine☐ Johnson counter☐ Ring counter

correct

Made by: Waqar Siddhu

Question No : 19 of 52

Marks: 1 (Budgeted Time 1 Min)

The power consumed by a flip-flop is defined by _____

Answer (Please select your correct option)

WWW.VirtualAcademyLive.com

☐ $P = I_{cc} \times R_{cc}$ ☐ $P = V_{cc} \times R_{cc}$ ☐ $P = V_{cc} \times I_{cc}$ ☐ $P = M_{cc} \times V_{cc}$

correct

Made by: Waqar Siddhu

Question No : 20 of 52

Marks: 1 (Budgeted Time 1 Min)

The minimum time required for the input logic levels to remain stable before the clock transition occurs is known as the _____

Answer (Please select your correct option)

WWW.VirtualAcademyLive.com

☐ Pulse Stability time (PST)☐ Set-up time☐ Hold time☐ Pulse Interval time

correct

Made by: Waqar Siddhu

Question No : 21 of 52

Marks: 1 (Budgeted Time 1 Min)

RCO Stands for _____

Answer (Please select your correct option)

WWW.VirtualAcademyLive.com

☐ Reconfiguration Counter Output

☐ Reconfiguration Clock Output

☐ Ripple Counter Output

☐ Ripple Clock Output

correct

Made by: Waqar Siddhu

Question No : 22 of 52

Marks: 1 (Budgeted Time 1 Min)

We have a digital circuit. Different parts of circuit operate at different clock frequencies (4MHZ, 2MHZ and 1MHZ), but we have a single clock source having a fix clock frequency (4MHZ), we can get help by using _____

Answer (Please select your correct option)

WWW.VirtualAcademyLive.com

☐ T-Flop-Flop

☐ S-R Flop-Flop

☐ D-Flop-Flop

☐ J-K Flop-Flop

correct

Made by: Waqar Siddhu

Question No : 23 of 52

Marks: 1 (Budgeted Time 1 Min)

The Sequential circuit, whose output is determined by the current state only is known as _____

Answer (Please select your correct option)

WWW.VirtualAcademyLive.com

☐ Moore Machine

correct

☐ Mealy Machine

☐ Counter

☐ Flip Flop

Made by: Waqar Siddhu

Question No : 24 of 52

Marks: 1 (Budgeted Time 1 Min)

State Machine is a generic name given to _____

Answer (Please select your correct option)

WWW.VirtualAcademyLive.com

☐

Sequential circuits

correct

☐

Combinational circuits

☐

Flip-flops

☐

Counters

Made by: Waqar Siddhu

Question No : 25 of 52

Marks: 1 (Budgeted Time 1 Min)

_____ is used to minimize the possible no. of states of a circuit.

Answer (Please select your correct option)

WWW.VirtualAcademyLive.com

☐

State assignment

correct

☐

State reduction

☐

Next state table

☐

State diagram

Made by: Waqar Siddhu

Question No : 26 of 52

Marks: 1 (Budgeted Time 1 Min)

_____ is used to simplify the circuit that determines the next state.

Answer (Please select your correct option)

WWW.VirtualAcademyLive.com

☐

State diagram

☐

Next state table

☐

State reduction

☐

State assignment


correct

Made by: Waqar Siddhu

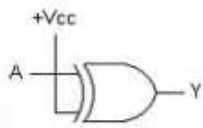Question No : 27 of 52

Marks: 1 (Budgeted Time 1 Min)

The output of this circuit is always _____.



Answer (Please select your correct option)

WWW.VirtualAcademyLive.com

1

☐

0

☐

A

☒


correct

 \bar{A} ☐

Made by: Waqar Siddhu

Question No : 28 of 52

Marks: 1 (Budgeted Time 1 Min)

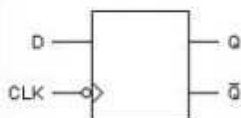

Which of the following statement is true regarding above block diagram ?

Answer (Please select your correct option)

WWW.VirtualAcademyLive.com

Triggering takes place on the negative-going edge of the CLK pulse

☐

Triggering takes place on the positive-going edge of the CLK pulse

☒

correct

Triggering can take place anytime during the LOW level of the CLK waveform

☐

Triggering can take place anytime during the LOW level of the CLK waveform

☐

Made by: Waqar Siddhu

Question No : 29 of 52

Marks: 1 (Budgeted Time 1 Min)

Which is not characteristic of a shift register?

Answer (Please select your correct option)

WWW.VirtualAcademyLive.com

Serial in/parallel in

☒

correct

Serial in/parallel out

☐

Parallel in/serial out

☐

Parallel in/parallel out

☐

Made by: Waqar Siddhu

Question No : 30 of 52

Marks: 1 (Budgeted Time 1 Min)

Assume that a 4-bit serial in/serial out shift register is initially clear. We wish to store the nibble 1100. What will be the 4-bit pattern after the second clock pulse? (Right-most bit first.)

Answer (Please select your correct option)

WWW.VirtualAcademyLive.com

☐ 1100☐ 0011☐ 0000

correct

☐ 1111

Made by: Waqar Siddhu

Question No : 31 of 52

Marks: 1 (Budgeted Time 1 Min)

A bidirectional 4-bit shift register is storing the nibble 1110. Its RIGHT/LEFT input is LOW. The nibble 0111 is waiting to be entered on the serial data-input line. After two clock pulses, the shift register is storing _____.

Answer (Please select your correct option)

WWW.VirtualAcademyLive.com

☐ 1110☐ 0111☐ 1000☐ 1001

correct

Made by: Waqar Siddhu

Question No : 32 of 52

Marks: 1 (Budgeted Time 1 Min)

Smallest unit of binary data is a _____.

Answer (Please select your correct option)

WWW.VirtualAcademyLive.com

☐ Bit

correct

☐ Nibble☐ Byte☐ Word

Made by: Waqar Siddhu

Question No : 33 of 52

Marks: 1 (Budgeted Time 1 Min)

The _____ of a ROM is the time it takes for the data to appear at the Data Output of the ROM chip after an address is applied at the address input lines

Answer (Please select your correct option)

WWW.VirtualAcademyLive.com

☐ Write Time

☐ Refresh Time

☐ Refresh Time

☐ Access Time

correct

Made by: Waqar Siddhu

Question No : 34 of 52

Marks: 1 (Budgeted Time 1 Min)

The high density FLASH memory cell is implemented using _____

Answer (Please select your correct option)

WWW.VirtualAcademyLive.com

☐ 1 floating-gate MOS transistor

correct

☐ 2 floating-gate MOS transistors

☐ 4 floating-gate MOS transistors

☐ 6 floating-gate MOS transistors

Made by: Waqar Siddhu

Question No : 35 of 52

Marks: 1 (Budgeted Time 1 Min)

The total amount of memory that is supported by any digital system depends upon _____

Answer (Please select your correct option)

WWW.VirtualAcademyLive.com

☐ The size of the address bus of the microprocessor

correct

☐ The organization of memory

☐ The structure of memory

☐ The size of decoding unit

Made by: Waqar Siddhu

Question No : 36 of 52

Marks: 1 (Budgeted Time 1 Min)

The voltage gain of the Inverting Amplifier is given by the relation _____

Answer (Please select your correct option)

WWW.VirtualAcademyLive.com

☐ $V_{out} / V_{in} = - R_f / R_i$

correct

☐ $V_{out} / R_f = - V_{in} / R_i$ ☐ $R_f / V_{in} = - R_i / V_{out}$ ☐ $R_f / V_{in} = R_i / V_{out}$

Made by: Waqar Siddhu

Question No : 37 of 52

Marks: 1 (Budgeted Time 1 Min)

The process of converting the analogue signal into a digital representation (code) is known as _____

Answer (Please select your correct option)

WWW.VirtualAcademyLive.com

☐ Strobing☐ Amplification☐ Quantization

correct

☐ Digitization

Made by: Waqar Siddhu

Question No : 38 of 52

Marks: 1 (Budgeted Time 1 Min)

A flash A/D converter uses :

Answer (Please select your correct option)

WWW.VirtualAcademyLive.com

☐ Counters☐ Flip-flops☐ Op-amps

correct

☐ An integrator

Made by: Waqar Siddhu

Question No : 39 of 52

Marks: 1 (Budgeted Time 1 Min)

_____ of a D/A converter is determined by comparing the actual output of a D/A converter with the expected output

Answer (Please select your correct option)

WWW.VirtualAcademyLive.com

☐

Resolution

☐

Accuracy

correct

☐

Quantization

☐

Missing Code

Made by: Waqar Siddhu

Question No : 40 of 52

Marks: 1 (Budgeted Time 1 Min)

In a binary-weighted D/A converter, the resistors on the inputs :

Answer (Please select your correct option)

WWW.VirtualAcademyLive.com

☐

Limit the power consumption

☐

Prevent loading on the source

☐

Determine the weights of the digital inputs

correct

☐

Determine the amplitude of the analog signal

Made by: Waqar Siddhu

Question No : 41 of 52


Marks: 2 (Budgeted Time 4 Min)

Identify the following quantities as analog and digital.

- a) Pressure in a bicycle tire
- b) Number of students in a class
- c) Speed of a car
- d) Temperature

Answer (Please click here to Add Answer)

WWW.VirtualAcademyLive.com

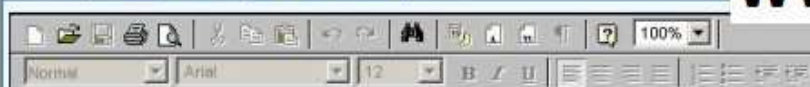

Made by: Waqar Siddhu

Question No : 42 of 52

Marks: 2 (Budgeted Time 4 Min)

What is strobing method?

Answer ([Please click here to Add Answer](#))

WWW.VirtualAcademyLive.com

Normal Arial 12 B I U

Made by: Waqar Siddhu

Question No : 43 of 52

Marks: 2 (Budgeted Time 4 Min)

Write down any two applications of shift registers.

Answer ([Please click here to Add Answer](#))

WWW.VirtualAcademyLive.com

Normal Arial 12 B I U

Made by: Waqar Siddhu

Question No : 44 of 52

Marks: 2 (Budgeted Time 4 Min)

How many address bits are required for a 2048-bit memory organized as a 256 x 8 memory?

Answer ([Please click here to Add Answer](#))

WWW.VirtualAcademyLive.com

Normal Arial 12 B I U

Made by: Waqar Siddhu

Question No : 45 of 52

Marks: 3 (Budgeted Time 6 Min)

Express each decimal number in binary as an 8-bit sign-magnitude number:

- (a) +29
- (b) -85

Answer ([Please click here to Add Answer](#))

WWW.VirtualAcademyLive.com



Made by: Waqar Siddhu


Question No : 46 of 52

Marks: 3 (Budgeted Time 6 Min)

How can we calculate the frequency of an unknown signal?

Answer ([Please click here to Add Answer](#))

WWW.VirtualAcademyLive.com

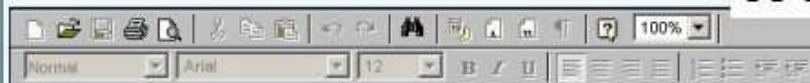

Made by: Waqar Siddhu


Question No : 47 of 52

Marks: 3 (Budgeted Time 6 Min)

Suppose a 2 bit up-down counter having states "A, B, C, D". The counter counts upward when $X=1$ and downward when $X=0$. Write down IF-THEN-ELSE statements to show how present states change to next states and previous states.

Answer ([Please click here to Add Answer](#))

WWW.VirtualAcademyLive.com

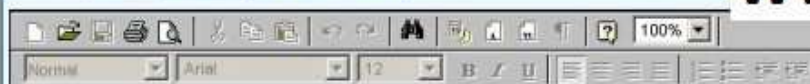

Made by: Waqar Siddhu

Answer ([Please click here to Add Answer](#))

WWW.VirtualAcademyLive.com




Made by: Waqar Siddhu

A 4-bit flash A/D converter is tested for faults. The resulting reconstructed analog output is shown below. Identify the problem and the most probable reason due to which this fault is occurred.



Answer: ([Please click here to Add Answer](#))

WWW.VirtualAcademyLive.com

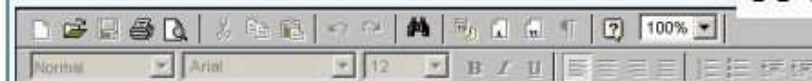


Made by: Waqar Siddhu

Convert the following caveman numbers into decimal numbers, perform all the steps.

- a) $\Omega \uparrow \Sigma$
b) $\uparrow \Delta \Delta \Sigma$

Answer ([Please click here to Add Answer](#))

WWW.VirtualAcademyLive.com

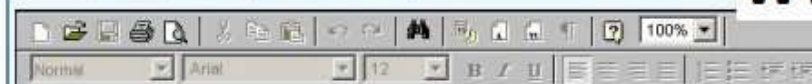

Made by: Waqar Siddhu

Question No : 50 of 52

Marks: 5 (Budgeted Time 10 Min)

You are given the Next-state table of a moor machine, using this information draw the state diagram of the machine.

Present State			Next State		
Q ₂	Q ₁	Q ₀	Q ₂	Q ₁	Q ₀
0	1	1	1	1	1
1	1	1	0	0	1
0	0	1	0	1	0

Answer ([Please click here to Add Answer](#))

WWW.VirtualAcademyLive.com

**Made by: Waqar Siddhu**


Question No : 51 of 52

Marks: 5 (Budgeted Time 10 Min)

Make block diagram of Rotate Left Operation of a shift register and explain its working.

Answer ([Please click here to Add Answer](#))

WWW.VirtualAcademyLive.com

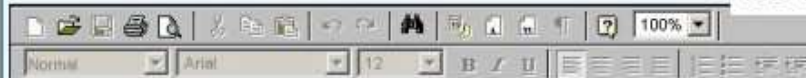**Made by: Waqar Siddhu**


Question No : 52 of 52

Marks: 5 (Budgeted Time 10 Min)

Analog to Digital converters exhibit different types of errors during their conversion operation. Explain at least two.

Answer ([Please click here to Add Answer](#))

WWW.VirtualAcademyLive.com

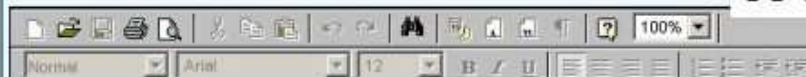**Made by: Waqar Siddhu**